

[illegible]

<b>Question Paper Code</b>	<b>13675</b>
----------------------------	--------------

**B.E. / B.Tech. - DEGREE EXAMINATIONS, APRIL / MAY 2025**

### Third Semester

**Electrical and Electronics Engineering**  
**20EEPC301 - ANALOG ELECTRONICS**

Regulations - 2020

Duration: 3 Hours

Max. Marks: 100

**PART - A (MCO) (10 × 1 = 10 Marks)**

**Answer ALL Questions**

PART - A (MCQ) (10 × 1 = 10 Marks)			
Answer ALL Questions			
	Marks	K-Level	CO
1. Which of the following FETs has a physical channel at zero gate bias? (a) Depletion-type MOSFET (b) Enhancement-type MOSFET (c) JFET (d) None of the above	1	K1	CO1
2. The input of an IGBT is controlled by: (a) Gate current (b) Collector current (c) Gate voltage (d) Base voltage	1	K1	CO1
3. Which amplifier class offers a compromise between linearity and efficiency? (a) Class A (b) Class B (c) Class C (d) Class AB	1	K1	CO2
4. The frequency of a Wien bridge oscillator is determined by: (a) Capacitor only (b) Inductor only (c) Resistor and capacitor (d) Feedback resistor	1	K1	CO2
5. Gain-bandwidth product of an Op-Amp is: (a) Constant for given Op-Amp (b) Variable with gain (c) Equal to input resistance (d) Maximum at low frequencies	1	K1	CO3
6. A differentiator circuit produces an output proportional to: (a) Integral of input (b) Rate of change of input (c) Square of input (d) Inverse of input	1	K1	CO3
7. In an ideal peak detector, the capacitor holds the peak voltage: (a) Indefinitely (b) For one cycle (c) Until the diode conducts again (d) Until reset manually	1	K1	CO4
8. In a DAC, the full-scale output corresponds to: (a) All bits = 0 (b) LSB = 1 (c) MSB = 0 (d) All bits = 1	1	K1	CO4
9. Which of the following components determines the timing interval in a 555 timer circuit? (a) The output voltage (b) The external resistor and capacitor (c) The trigger voltage (d) The power supply	1	K1	CO5
10. A common problem with linear regulators is: (a) Low efficiency due to heat dissipation (b) High ripple voltage (c) Inconsistent output voltage under load (d) High frequency noise	1	K1	CO5

**PART - B (12 × 2 = 24 Marks)**

**Answer ALL Questions**

11. Compare FET and BJT.	2	K2	CO1
12. Show the transfer characteristic for n-channel depletion type MOSFET.	2	K1	CO1
13. Define the term Gate in IGBT.	2	K1	CO1
14. Demonstrate the impact of cross over distortion in an amplifier.	2	K2	CO2
15. Illustrate the need of complementary symmetry amplifiers.	2	K2	CO2
16. Outline the features of crystal oscillator.	2	K2	CO2
17. A 100 pF capacitor has a maximum charging current of 100 micro amps. Calculate its slew rate.	2	K2	CO3

*K1 – Remember; K2 – Understand; K3 – Apply; K4 – Analyze; K5 – Evaluate; K6 – Create*

13675

- |   |   |    |     |
|---|---|----|-----|
| 18. For a non-inverting amplifier using an op-amp, assume $R_1 = 470 \text{ ohm}$ and $R_2 = 4.7K \text{ ohm}$ . Calculate the closed loop voltage gain of the amplifier. | 2 | K2 | CO3 |
| 19. Summarize the applications of an instrumentation amplifier.   | 2 | K2 | CO4 |
| 20. Choose the number of comparators required for realizing an 8 bit ADC.   | 2 | K2 | CO4 |
| 21. Summarize any two applications of 555 Timer in Monostable mode.   | 2 | K2 | CO5 |
| 22. Infer the principle of switching regulator.   | 2 | K2 | CO5 |

**PART - C ( $6 \times 11 = 66$  Marks)**

Answer ALL Questions

- |   |    |    |     |
|---|----|----|-----|
| 23. a) Illustrate the circuit of emitter coupled BJT differential amplifier, and derive expressions for differential gain, common mode gain and CMRR. | 11 | K2 | CO1 |
|---|----|----|-----|

**OR**

- |   |    |    |     |
|---|----|----|-----|
| b) Draw the circuit diagram of a common drain MOSFET amplifier. Derive the expression for its voltage gain, input resistance and output resistance. | 11 | K2 | CO1 |
|---|----|----|-----|

- |  |    |    |     |
|--|----|----|-----|
| 24. a) Infer about complementary symmetry class B amplifier and obtain its efficiency. | 11 | K2 | CO2 |
|--|----|----|-----|

**OR**

- |  |    |    |     |
|--|----|----|-----|
| b) Explain the RC phase shift oscillator with a neat diagram by using BJT and also derive the condition for oscillation. | 11 | K2 | CO2 |
|--|----|----|-----|

- |   |    |    |     |
|---|----|----|-----|
| 25. a) Interpret the frequency response of op-amp. Give the frequency compensation techniques adopted in op-amps. | 11 | K2 | CO3 |
|---|----|----|-----|

**OR**

- |  |    |    |     |
|--|----|----|-----|
| b) With the help of circuit diagrams explain the operation of I to V and V to I converters and their applications. | 11 | K2 | CO3 |
|--|----|----|-----|

- |   |    |    |     |
|---|----|----|-----|
| 26. a) Explain the Instrumentation amplifier using 3-Op-Amp and derive expression for overall gain. | 11 | K2 | CO4 |
|---|----|----|-----|

**OR**

- |  |    |    |     |
|--|----|----|-----|
| b) Explain Successive Approximation ADC and give its advantages and disadvantages. | 11 | K2 | CO4 |
|--|----|----|-----|

- |   |    |    |     |
|---|----|----|-----|
| 27. a) Illustrate the functional block diagram of a 723 IC regulator and make the necessary changes to make it a low voltage regulator. | 11 | K2 | CO5 |
|---|----|----|-----|

**OR**

- |  |    |    |     |
|--|----|----|-----|
| b) With neat block diagram explain the working of function generator IC8038. | 11 | K2 | CO5 |
|--|----|----|-----|

- |   |   |    |     |
|---|---|----|-----|
| 28. a) (i) Explain the operation of R-2R D/A converter.                                       | 6 | K2 | CO4 |
| (ii) Explain the operation of a free running oscillator using IC555 with necessary waveforms. | 5 | K2 | CO5 |

**OR**

- |  |   |    |     |
|--|---|----|-----|
| b) (i) Demonstrate the operation of sample and hold circuit using IC741. | 6 | K2 | CO4 |
| (ii) Classify the various types of Fixed voltage regulators.             | 5 | K2 | CO5 |