

[illegible]

Question Paper Code	13525
----------------------------	--------------

B.E. / B.Tech. - DEGREE EXAMINATIONS, APRIL / MAY 2025

Third Semester

Electrical and Instrumentation Engineering

20EIPC303 - ANALOG ELECTRONIC CIRCUITS

Regulations - 2020

Duration: 3 Hours

Max. Marks: 100

PART - A (MCQ) (10 × 1 = 10 Marks)

Answer ALL Questions

PART - A (MCQ) (10 × 1 = 10 Marks)		Marks	K – Level	CO
Answer ALL Questions				
1. In a Common Emitter (CE) configuration of a BJT, the output is taken across which terminals?		1	K1	CO1
(a) Base and Emitter	(b) Collector and Base			
(c) Collector and Emitter	(d) Base and Collector			
2. What is the main function of a UJT (Unijunction Transistor)?		1	K1	CO1
(a) High-frequency amplification	(b) Voltage regulation			
(c) Oscillation and triggering	(d) Power switching			
3. Which of the following FET amplifier configurations offers high input impedance and is typically used as a buffer?		1	K1	CO2
(a) Common Gate (CG)	(b) Common Source (CS)			
(c) Common Drain (CD)	(d) Differential			
4. Which of the following is a major drawback of Class B amplifiers that Class AB aims to reduce?		1	K1	CO2
(a) Low input impedance	(b) High power dissipation			
(c) Crossover distortion	(d) Large size			
5. What is one major advantage of using negative feedback in an amplifier?		1	K1	CO3
(a) Reduces input impedance	(b) Increases distortion			
(c) Improves gain stability and reduces noise	(d) Decreases bandwidth			
6. Which of the following is a necessary condition for oscillation in a feedback circuit?		1	K1	CO3
(a) Feedback factor must be zero				
(b) The loop gain must be less than one				
(c) The total phase shift around the loop must be 180°				
(d) Loop gain must be unity and total phase shift must be 0° or 360°				
7. Which of the following is a key characteristic of an ideal operational amplifier (op-amp)?		1	K1	CO4
(a) Infinite output impedance	(b) Infinite bandwidth and infinite open-loop gain			
(c) High input current	(d) Low common-mode rejection ratio			
8. The purpose of a sample and hold (S/H) circuit using an op-amp is to:		1	K1	CO4
(a) Differentiate the input signal				
(b) Filter high-frequency noise				
(c) Maintain a constant output voltage during sampling intervals				
(d) Generate square waves				
9. Which IC is commonly used for generating sine, square, and triangular waveforms over a wide frequency range?		1	K1	CO5
(a) IC741	(b) IC555			
(c) IC8038	(d) LM317			
10. In astable mode, the 555 timer generates:		1	K2	CO5
(a) A single pulse	(b) A continuous square wave			
(c) A sine wave	(d) A ramp signal			

PART - B (12 × 2 = 24 Marks)

Answer ALL Questions

- | | | | |
|--|---|----|-----|
| 11. What is the purpose of biasing in BJT amplifiers? | 2 | K1 | CO1 |
| 12. What is the function of the base region in a BJT transistor? | 2 | K1 | CO1 |
| 13. What is the significance of diffusion and transition capacitance in a PN junction diode? | 2 | K2 | CO1 |
| 14. What is meant by crossover distortion in Class B power amplifiers? | 2 | K1 | CO2 |
| 15. State the basic difference between JFET and MOSFET. | 2 | K2 | CO2 |
| 16. What is the role of source resistance in a common drain (CD) amplifier? | 2 | K1 | CO2 |
| 17. State the basic principle behind the working of a Wien Bridge Oscillator. | 2 | K1 | CO3 |
| 18. Differentiate between voltage-series and current-shunt feedback topologies. | 2 | K2 | CO3 |
| 19. List the applications of instrumentation amplifier. | 2 | K1 | CO4 |
| 20. What is the need for clipper and clamper circuits? | 2 | K2 | CO4 |
| 21. Differentiate between astable and monostable mode of operation. | 2 | K2 | CO5 |
| 22. List few applications of LM317. | 2 | K1 | CO5 |

PART - C (6 × 11 = 66 Marks)

Answer ALL Questions

- | | | | |
|---|----|----|-----|
| 23. a) Draw the structure of a PN junction diode and explain its V-I characteristics under forward and reverse bias conditions. | 11 | K2 | CO1 |
| OR | | | |
| b) Discuss the different types of biasing techniques used in BJT amplifiers. Explain the need for stabilization and thermal runaway prevention. | 11 | K2 | CO1 |
| 24. a) With a neat diagram explain the construction and working of JFET and MOSFET. | 11 | K2 | CO2 |
| OR | | | |
| b) Explain the operation and characteristics of a Class B push-pull amplifier. How can a crossover distortion be minimized. | 11 | K2 | CO2 |
| 25. a) With neat circuit diagram explain the construction and working principle of a phase shift oscillator. | 11 | K2 | CO3 |
| OR | | | |
| b) Explain the different types of feedback configurations with suitable diagrams. State the advantages of negative feedback in amplifiers. | 11 | K2 | CO3 |
| 26. a) Explain the function of op-amp based clipper and clamper circuits. Use diagrams to show how input waveforms are modified by these circuits. | 11 | K2 | CO4 |
| OR | | | |
| b) Explain the working of an instrumentation amplifier using op-amps. List its advantages and applications in measurement systems. | 11 | K2 | CO4 |
| 27. a) Draw and explain the functional block diagram of a 555 timer IC. Describe how it operates in astable mode with a suitable timing diagram and waveform. | 11 | K2 | CO5 |
| OR | | | |
| b) Explain the function and operation of the IC8038 function generator. Illustrate the waveform outputs and the internal block diagram to support your explanation. | 11 | K2 | CO5 |
| 28. a) i) Explain the working principle of op-amp based monostable multivibrator. | 6 | K2 | CO4 |
| ii) Describe the internal block diagram and working of the LM317 adjustable voltage regulator. | 5 | K2 | CO5 |

OR

- b) i) Explain the operation of an op-amp based differentiator circuit.
ii) Explain the operation of the IC723 voltage regulator.

6 K2 CO4

5 K2 CO5