

21. How does a thermocouple works?
 22. What is the necessity of earthing?


2 K1 CO5
 2 K1 CO5

PART - C ($6 \times 11 = 66$ Marks)

Answer ALL Questions

23. a) Infer the current in all branches by using mesh matrix method.


11 K2 CO1

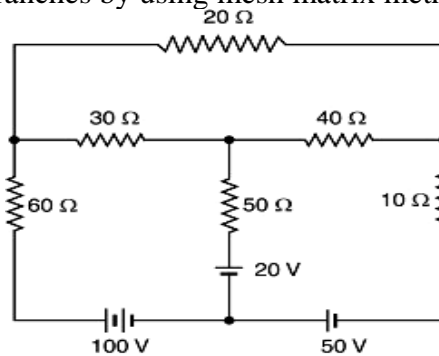

OR


- b) Show the branch currents of the network by using mesh analysis or Nodal analysis.

11 K2 CO1

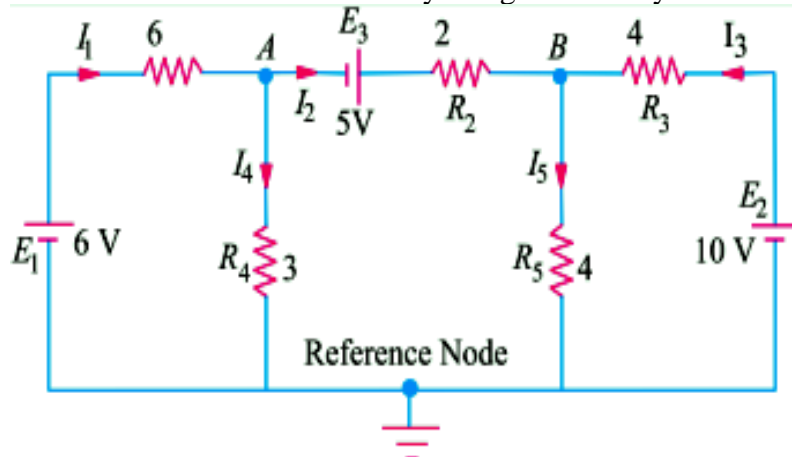

24. a) Make use of Norton's equivalent circuit and solve for load voltage and load current.


11 K3 CO2

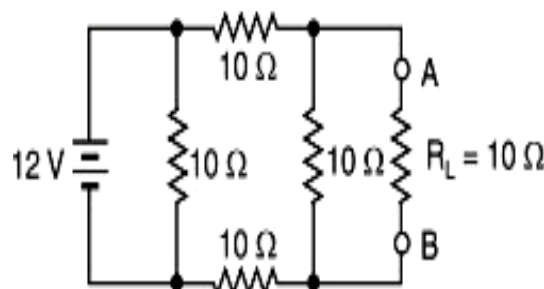

OR

- b) Identify the current in the $R = 1$ ohm by superposition theorem.

11 K3 CO2

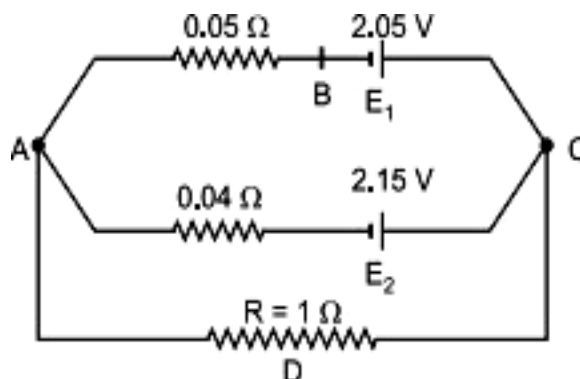

25. a) Explain the operation of AC circuit containing R only with equations for phase angle, phasor diagram, power and also draw the power curve. 11 K2 CO3
- OR**
- b) A Coil having a resistance of 7ohm and an inductance of 31.8 mH is connected in 230 V, 50 Hz. Interpret (i) Circuit current (ii) Phase angle (iii) Power factor (iv) Power consumed and (v) Voltage drop across resistor and inductor. 11 K2 CO3
26. a) Explain about electric field and electric intensity. 11 K2 CO4
- OR**
- b) Outline about the charging of capacitor with neat diagram. 11 K2 CO4
27. a) Explain the construction and working principle of single phase wattmeter. 11 K2 CO5
- OR**
- b) Illustrate the working of thermocouple with a functional block diagram. 11 K2 CO5
28. a) (i) Classify the types of transformer with neat diagram. 6 K2 CO4
(ii) Explain the working and principle of PMMC. 5 K2 CO5
- OR**
- b) (i) Summarize the transformation ratio of the transformer. 6 K2 CO4
(ii) Explain the working of Moving Iron Instrument. 5 K2 CO5