



**PART - B (12 × 2 = 24 Marks)**


Answer ALL Questions

- |  |   |    |     |
|--|---|----|-----|
| 11. State Ohm's law. Mention the limitations of ohm's law?   | 2 | K1 | CO1 |
| 12. Two resistors $4\Omega$ and $6\Omega$ are connected in parallel. The total current flowing through the resistors is 5A. Find the current flowing through each resistor.  | 2 | K2 | CO1 |
| 13. Define real power, reactive power, and apparent power in AC circuits.  | 2 | K1 | CO2 |
| 14. What is the average value of a sinusoidal waveform over one full cycle?  | 2 | K1 | CO2 |
| 15. List out the applications of maximum power transfer theorem.   | 2 | K1 | CO3 |
| 16. A load is connected to a network of the terminals to which load is connected with $R_{th}=10\Omega$ and $V_{th}=40V$ . Calculate the maximum power supplied to the load. | 2 | K2 | CO3 |
| 17. Define the term 'time constant'.   | 2 | K1 | CO4 |
| 18. Define the term forced response of a circuit.  | 2 | K1 | CO4 |
| 19. Find the maximum possible mutual inductance of two Inductively coupled circuits with self inductance $L_1=16\text{ H}$ and $L_2=4\text{H}$ .                             | 2 | K2 | CO5 |
| 20. Define bandwidth of the resonant circuit.  | 2 | K1 | CO5 |
| 21. Compare between balanced supply and unbalanced load.   | 2 | K2 | CO6 |
| 22. List out the advantages of 3-phase system over 1 phase system.   | 2 | K1 | CO6 |

**PART - C (6 × 11 = 66 Marks)**


Answer ALL Questions

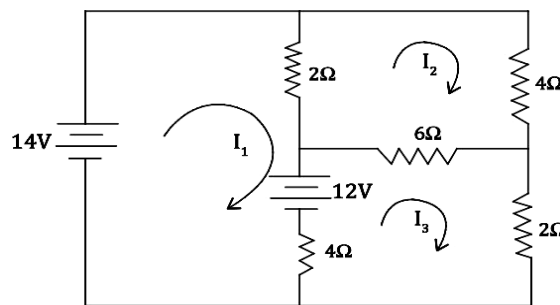23. a) Solve the Loop currents  $I_1$ ,  $I_2$  and  $I_3$  by using Mesh loop analysis as shown in Fig. 11 K3 CO1




OR

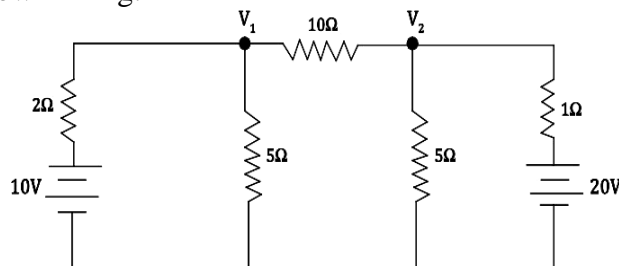- b) Make use of Nodal Voltages analysis method, derive and formulate the value of  $V_1$ , and  $V_2$  as shown in Fig. 11 K3 CO1



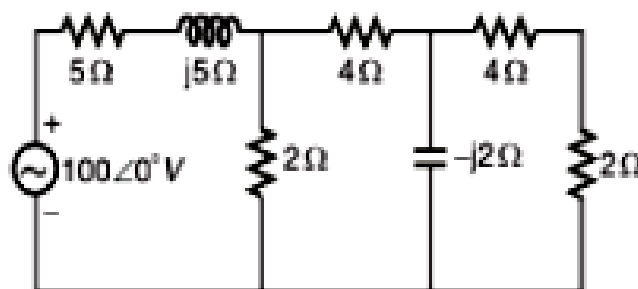
24. a) Solve the currents in various branches of the circuit shown in Figure using mesh analysis. 11 K3 CO2



OR


- b) Develop the expressions for RMS value, average value, Form Factor and Peak Factor of a sinusoidal voltage. 11 K3 CO2

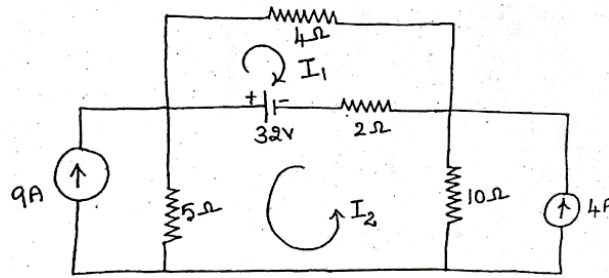25. a) Solve the current through  $5\ \Omega$  resistor using superposition theorem, in the circuit shown in Fig. 11 K3 CO3




OR

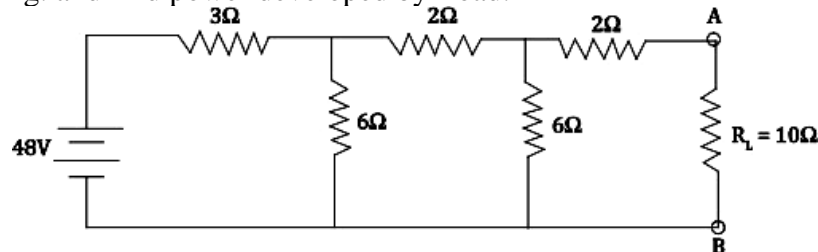- b) Make use of Thevenin's theorem, Evaluate the current through  $R_L = 10\ \Omega$  as shown in Fig. and find power developed by Load. 11 K3 CO3



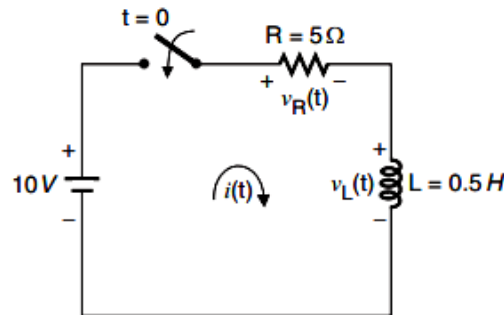26. a) In the RL circuit of Fig. 1, the switch is closed at  $t = 0$ . Solve the current  $i(t)$  and the voltage across resistance and inductance. 11 K3 CO4



OR

- b) Develop the transient response of series R-L circuit, with AC input, using Laplace transform and also sketch the transient response curve. 11 K3 CO4

27. a) A series circuit with  $R=10\ \Omega$ ,  $L=0.1\text{H}$  and  $C=50\ \mu\text{F}$  has an applied voltage  $V=50\angle 0^\circ\text{ V}$  with a variable frequency. Find (1) the resonant frequency (2) the value of frequency at which maximum voltage occurs across inductor (3) value of frequency at which maximum voltage occurs across capacitor (4) quality factor of coil. 11 K3 CO5

OR

- b) Develop the mutual inductance and the coupling coefficient of the transformer with necessary illustration. 11 K3 CO5

28. a) A balanced Star connected load of  $(4+j3)\ \Omega$  / Phase is connected to a 3-Phase, 230V, 50Hz Supply. Evaluate (i) Line Current (ii) Power Factor (iii) Reactive volt Amperes (iv) Power in VA. 11 K3 CO6

OR

- b) Construct the power and power factor measuring in the three phase by two wattmeter method. 11 K3 CO6