

Reg. No.																			
----------	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code	12317
---------------------	-------

M.E. / M.Tech. - DEGREE EXAMINATIONS, NOV / DEC 2023

First Semester

M.E. - Embedded Systems Technologies

20PESPC101 - ADVANCED DIGITAL PRINCIPLES AND DESIGN

(Regulations 2020)

Duration: 3 Hours

Max. Marks: 100

PART - A (10 × 2 = 20 Marks)

Answer ALL Questions

*Marks,
K-Level, CO*

1. Recollect the Characteristic equation and table of JK flip flop. *2,K1,CO1*
2. Recall the excitation table for JK flipflop. *2,K1,CO1*
3. Bring out the importance of state reduction. *2,K2,CO2*
4. Give the reduced state table in the design of sequential circuits for minimizing the hardware. *2,K2,CO2*


Present state	Next state	Next state	Output Z1	Outputz2
a	d	b	0	0
b	e	a	0	0
c	g	f	0	1
d	a	d	1	0
e	a	b	1	0
f	d	b	0	0
g	a	e	1	0

5. Bring out the difference between the stuck at 0 and stuck at 1 fault. *2,K2,CO3*
6. State the importance of Built in Self Test. *2,K1,CO3*
7. Differentiate between PAL and PLA. *2,K2,CO4*
8. List the important features of Xilinx FPGA family. *2,K1,CO4*
9. Outline the advantage of reconfigurable logic designs. *2,K2,CO5*
10. State the advantages of CLBs. *2,K1,CO5*

PART - B (5 × 13 = 65 Marks)

Answer ALL Questions

 11. a) Illustrate the Transition table, Excitation table, state table and state diagram for the following synchronous sequential circuit and *13,K2,CO1*



OR

- b) An Asynchronous sequential circuit is given by the following excitation and output function

$$Y_1 = x_1x_2 + x_1y_2 + x_2y_1$$

$$Y_2 = x_2 + x_1y_1y_2 + x_1y_1$$

$$Z = x_2 + y_1$$

- (i) Draw the logic diagram of the circuit.

- (ii) Derive the transition table and output map.

8,K2,CO1
5,K2,CO1

12. a) In the design a network produces a 1 if and only if the current input and the previous 3 inputs correspond to either of the sequence 1001 or 0110. The one output occurs at the time of fourth input of the recognized sequence. Output of 0 is to be produced at all other times and the sequences are allowed to overlap. Give the state diagram and the reduced state table.

13,K3,CO2

OR

- b) Design a 0110/1001 sequence detector. Give the state diagram and the reduced state table.

13,K3,CO2


13. a) Derive the primitive flow table and state Diagram for the system with inputs X and Y and output Z. Initially both inputs and outputs are 0. If X = 1 and Y = 0 output Z=1. When X = 0 and Y = 1 output Z=0. If X = Y = 0 or X = Y = 1 then output Z has no change. The logic system has edge triggered input and any static inputs will not have any effect on the system output Z.

13,K2,CO3

OR

- b) For a given diagram, find a-test using kohavi algorithm to find faults in x1.

13,K2,CO3

 

14. a) Discuss in detail the interconnects and memory architecture of Xilinx 2000 with necessary diagram. 13,K2,CO4

OR

- b) Explain in detail the Programmable Electrically Erasable Logic and the different Programming Techniques. 13,K2,CO4

15. a) A combinational logic circuit is defined by the function given below. 13,K2,CO5
Implement the circuit using Programmable Array Logic.

$$F(R,S,T,U) = \sum(3,5,7,14,15)$$

$$G(R,S,T,U) = \sum(3,4,5,7,10)$$

OR

- b) Implement the following Boolean function using Programmable Logic Array. 13,K2,CO5

$$W(A,B,C,D) = \sum(0,2,6,7,8,9,12,13)$$

$$X(A,B,C,D) = \sum(0,2,6,7,8,9,12,13,14)$$

$$Y(A,B,C,D) = \sum(2,3,8,9,10,12,13)$$

$$Z(A,B,C,D) = \sum(1,3,4,6,9,12,14)$$

PART - C (1 × 15 = 15 Marks)

16. a) Analyze the operation of 4:1 Multiplexer and compare the VHDL programming model of the same. 15,K4,CO6

OR

- b) Compare and contrast the structural and behavioral modeling of VHDL with suitable examples. 15,K4,CO6