

Reg. No.																			
----------	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code	12599
---------------------	-------

B.E. / B.Tech. - DEGREE EXAMINATIONS, APRIL / MAY 2024

Sixth Semester

Electronics and Communication Engineering

EC8651 - TRANSMISSION LINES AND RF SYSTEMS

Regulations - 2017

(Use of Smith Chart is permitted)

Duration: 3 Hours

Max. Marks: 100

PART - A (10 × 2 = 20 Marks)

Answer ALL Questions

	Marks	K- Level	CO
1. Define propagation constant.	2	K1	CO1
2. Find the reflection coefficient of a 50 ohm transmission line when it is terminated by load of $60+j40$ ohm.	2	K2	CO1
3. What is standing wave ratio?	2	K1	CO2
4. Write the conditions to be satisfied by a dissipationless line.	2	K2	CO2
5. Give two applications of smith chart?	2	K1	CO3
6. What is the use of eighth wave line?	2	K1	CO3
7. What is degenerate mode in rectangular waveguide?	2	K1	CO4
8. Calculate the cutoff wavelength of a rectangular waveguide whose inner dimensions are $a=2.3$ cm and $b=1.03$ cm operating at TE ₁₀ mode.	2	K2	CO5
9. List out the types of Power Amplifiers.	2	K1	CO6
10. What are the advantages of microwave transistors?	2	K1	CO6

PART - B (5 × 13 = 65 Marks)

Answer ALL Questions

11. a) Obtain the general transmission line equation for the Voltage and current at any point on a transmission line.	13	K1	CO1
OR			
b) Explain in detail about the primary constants and secondary constants of a transmission line and bring the relation between them	13	K2	CO1
12. a) Calculate the input impedance of the dissipation less line, also deduce the input impedance of an open and short circuited dissipation less line.	13	K2	CO2
OR			
b) i) List out the parameters of open wire and coaxial cable at High frequency.	6	K1	CO2
ii) A certain transmission line, working at radio frequencies, has	7	K3	CO2

K1 – Remember; K2 – Understand; K3 – Apply; K4 – Analyze; K5 – Evaluate; K6 – Create

12599

following constants $L = 9$ and $C = 16$ PF/m. The line is terminated in a resistive load of 1000. Calculate the reflection co-efficient and standing wave ratio.

13. a) An antenna with impedance of $40+j30\Omega$ is to be matched to a 100Ω lossless line with a short circuited stub. Determine the following using Smith chart. (i) The required stub admittance (ii) The distance between the stub and antenna (iii) the stub length (iv) the standing wave ratio on each of the system and operating frequency 500 MHz. 13 K3 CO3

OR

- b) Derive the expression of quarter wave line. How a quarter wave line can be used as impedance matching. List out the different methods of impedance matching. 13 K3 CO3
14. a) Express the field expression for TE wave propagation in rectangular waveguide stating the necessary assumptions. 13 K2 CO4
- OR**
- b) A standard air filled rectangular waveguide with dimensions $a = 8.5$ cm and $b = 4.3$ cm is fed by a 4 GHz carrier from co-axial cable. Calculate if a TE₁₁ mode will be propagated. If so calculate phase velocity and group velocity. 13 K3 CO5

15. a) With reference to RF transistor amplifier, explain the considerations for stability and gain. 13 K3 CO6

OR

- b) Explain with necessary diagrams the various types of mixers and its principle of operation. 13 K2 CO6

PART - C (1 × 15 = 15 Marks)

16. a) An antenna with impedance of $40+j30\Omega$ is to be matched to a 100Ω lossless line with a short circuited stub. Determine the following using Smith chart. (i) The required stub admittance (ii) The distance between the stub and antenna (iii) the stub length (iv) the standing wave ratio on each of the system and operating frequency 500 MHz. 15 K3 CO3

OR

- b) Describe the impedance matching technique using single stub and obtain the expression for the stub location and stub length. 15 K3 CO3